

Arduino

ez Serial/Parallel IC Library (SIPO8) ~ Tutorial 4

A Tutorial to Consolidate Understanding
& Use of the ez Serial/Parallel IC Library
(SIPO8)

Tutorial 4
~ Cascading SIPOs ~

Author: R D Bentley, Stafford, UK.
Date: May 2021
Version: 1.00

Warranties & Exceptions

This document and its content are in the public domain
and may be used without restriction and without warranty.

Change Record

Version	Date	Change
1.00	May 2021	Initial version published

Audience

To fully understand and make good use of this User Guide and the capabilities of the `<ez_SIPO8_lib>` library, the reader should already be familiar with 8bit serial/parallel ICs (SIPOs), such as the [74HC595](#)¹ IC. Familiarity with wiring these ICs and driving them with suitable Arduino code, for example the standard `shiftOut` function, provides an excellent basis on which to build and develop sophisticated and innovative solutions through the use of the `<ez_SIPO8_lib>` library.

¹ Throughout this User Guide links to internet resources will be provided where further information may be considered to be helpful. In so doing, there is no intention to promote any supplier or product.

Contents

Warranties & Exceptions.....	2
Change Record.....	2
Audience.....	2
Introduction to the Tutorial	4
Objectives.....	4
Steps.....	4
Kit List.....	4
74HC595 Orientation and Pin Outs	4
UNO / SIPO Interface Pin Configuration	5
Connecting It All Together.....	5
The Code/Sketch.....	7

Introduction to the Tutorial

In this tutorial we will look at configuring and driving two 8bit SIPO ICs, the 74HC595 IC, in a single cascade, to provide 16 outputs in a single SIPO bank.

(If you have not already done so, download the SIPO8 User Guide from [github](#).)

Objectives

In this tutorial we shall build on what we have learned from previous tutorials and concern ourselves with creating a SIPO environment in which we can apply further basic principles to drive a cascade of two SIPO ICs, comprising a single SIPO bank. In particular we shall learn:

1. how we can wire up and cascade two 74HC595 ICs (SIPO ICs), as a single SIPO bank, to the microcontroller
2. how we are able to use some of the SIPO8 library functions/methods to drive the cascaded SIPO bank
3. how we can extend the two SIPO cascade model to any number of connected SIPOs in a single SIPO bank cascade
4. witness the outputs of the sketch - shifting LED patterns and serial monitor SIPO data

Steps


Kit List

Gather together the following components:

Components	Number	Comment
Arduino UNO	1	The design uses an Arduino UNO, but any suitable microcontroller (Arduino or clone, e.g. Elegoo) will do, providing it is able to support the pin out requirements for driving the SIPO interface and power requirements.
Breadboard(s)	1/2	One or two breadboards to fit 2 x ICs, resistors and LEDs
74HC595 IC	2	8bit SIPO ICs, or other clone providing it is genuinely 'plug-compatible'.
LEDs	16	Whatever you have around.
Resistors, 220 ohm	16	One per LED. Use 220 ohm resistors and ignore the suggested 180 ohm values in the wiring diagrams.
Connecting wires	Lots	Short/long or breadboard wire connectors, whatever suits. Breadboard bridging wires are helpful if you have any.

74HC595 Orientation and Pin Outs

 Which end is which? Well, notice that the 74HC595 has a notch at one end, here at the top of the diagram. Pin numbering starts at 1 at the top left and continues down and then around the bottom of the IC rising to the top right hand side:



Pin Outs 1 - 74HC595

For this tutorial we shall be using an addition IC pin, Q_H' (serial out) on the first IC, to link to the second SIPO in our two SIPO cascade.

UNO / SIPO Interface Pin Configuration


Every bank of SIPO ICs you connect to the microcontroller requires a 3-wire digital interface. The table below suggests pin mapping between the microcontroller and the SIPO IC for this tutorial, but you may choose what microcontroller digital pins you wish. If you do choose different pins then be sure to alter the sketch `create_bank` call.

UNO Pin	SIPO Pin(s)	Comment
8	14	SIPO Data Pin
9	12	SIPO Latch Pin
10	11	SIPO Clock Pin
+5v	10, 16	Power to the SIPO
GND	8, 13	Return ground (0v)

Note that we use the same microcontroller digital pins for the SIPO IC cascade interface - no change required.

Connecting It All Together

 Using the following diagram, wire up all of the components, taking care to get the output/input connections correct:



Wiring Scheme 1 - Cascaded SIPOs, 16 outputs

Take time to layout your components and try and keep to a logical order. It is very easy to get out of step and make incorrect connections. The illustration above provides all of the information required to complete the wiring up process. I recommend the following approach:

1. on the breadboard, position your two SIPO ICs in a convenient position and straddling the central break line. Orientate each SIPO correctly, note the notch indicating which end is which and where pin 1 starts
2. next position your LEDs and resistors on the same or another breadboard, convenient for wiring up to the SIPO output pins (remember, the SIPO ICs have all but one of their outputs on one side - pins 1 - 7)
3. now make all of the ground connections, followed by the power connections, see figure 1, above.
4. then connect all other pins together including the LEDs as per figure 1, above, except the 3-wire connections to the microcontroller
5. now carefully inspect your work and when happy
6. connect the 3-wire interface wires as per UNO / SIPO Interface Pin Configuration table above. Top tip - colour code the 3-wire connectors, e.g. SIPO pin 14 - data/red, SIPO pin 12 - latch/white, SIPO pin 11 - clock/green, or any other colouring of your choice. This makes it easy to recall which wire is which when you connect to the microcontroller.

As a further tip, try and use breadboard connecting bridge cables where you can, it keeps things looking tidier. But, you should now be all good to go?

The Code/Sketch

Now that is done, let's look at a simple sketch to play around with the 75HC595.

Using the Arduino IDE, start with a new sketch and enter the following (download from [github](#)):

```
// Tutorial 4 - use of ez_SPI8 library,
// 2 x physical SIPOs, cascaded into a single SIPO bank
//
// Ron D Bentley, Stafford, UK
// April 2021
//
// This example and code is in the public domain and
// may be used without restriction and without warranty.
//

#include <ez_SIPO8_lib.h>

int bank_id;

#define Num_SIPOs    2
#define Num_timers    0

// initiate the class for the tutorial
SIPO8 my_SIPOs(Num_SIPOs, Num_timers);

void setup() {
    Serial.begin(9600);
    // create a single bank of required number of SIPOs in the bank,
    // params are: data pin, clock pin, latch pin, number of SIPOs this bank
    bank_id = my_SIPOs.create_bank(8, 10, 9, 2);
    if (bank_id == create_bank_failure) {
        my_SIPOs.print_SIPO_data();
        Serial.println(F("failed to create bank"));
        Serial.flush();
        exit(0);
    }
    // print the bank data for confirmation/inspection
    my_SIPOs.print_SIPO_data();
}

// patterns to be xferred / shifted out to the SIPO bank
#define num_patterns 7
uint8_t patterns[num_patterns] = { // starting patterns
    0b11111111,
    0b00001111,
    0b00110011,
    0b01010101,
    0b11000011,
    0b01000010,
    0b00111100
};

void loop() {
    // scroll through every SIPO bank and assert the given pattern to every
    // SIPO defined by the bank.
    do {
        // setup each pattern in turn
        for (uint8_t pattern = 0; pattern < num_patterns; pattern++) {
            // perform 2 passes for each pattern - 1st, as defined, 2nd inverted
            for (uint8_t cycle = 0; cycle < 2; cycle++) {
                // consider each SIPO in this 2 SIPO cascaded bank
                for (uint8_t sipo = 0;
```

```
        sipo < my_SIPOs.SIPO_banks[bank_id].bank_num_SIPOs;
        sipo ++) {
            // set all pins of this sipo in this bank_id
            my_SIPOs.set_bank_SIPO(bank_id, sipo, patterns[pattern]);
        }
        // update physical SIPOs for this bank_id
        my_SIPOs.xfer_bank(bank_id, MSBFIRST);
        delay(500); // wait a little time so we can see the results
        // invert current pattern byte for next pass
        patterns[pattern] = ~patterns[pattern];    }
    }
} while (true);
}
```

Compile the sketch and upload. You should now see the LEDs performing the preset binary patterns.

Points to note:

1. there are few SIPO8 library functions/methods utilised in the sketch, `create_bank`, `set_bank_SIPO`, and `xfer_bank`. The sketch does include a `print_SIPO_data` function call but this is not needed and only included so you are able to verify your setup data (see below example)
2. we make use of a native SIPO control structure data value - `my_SIPOs.SIPO_banks[bank_id].bank_num_SIPOs`, although we could have simply stated "2" as the number of SIPOs within the SIPO bank. This is demonstrated here as a help for future projects where you may be dealing with many SIPO banks each with many SIPO ICs - it makes the method transparent

Finally, check the serial monitor, it should look like this:

```
SIPO global values:
pins_per_SIPO    = 8
max_SIPOs        = 2
bank_SIPO_count  = 2
num_active_pins  = 16
num_pin_status_bytes = 2
next_free bank   = all SIPOs used
Number timers    = 0

Bank data:
bank = 0
  num SIPOs =      2
  latch_pin =      9  clock_pin =    10  data_pin  =      8
  low_pin   =      0  high_pin  =    15
```

Note the helpful details that `print_SIPO_data()` function can provide - very useful during development and debugging.

Have a play around varying the patterns, reducing the sketch to a single SIPO bank, adding more SIPO ICs to your two SIPO bank cascade, adding more banks, etc. The most difficult aspect of using SIPO ICs is the number of cables/connections needed - a tidy mind helps.

That is the end of Tutorial 4.